

EE 105 Spring 2026

Prelab Worksheet 3: Diodes, Rectifiers, Optical Transceivers

Name(s): _____

Lab Section: _____

Submit this worksheet to Gradescope before your lab section the week it is due.

1

Expected Output:

2

$V_s =$ _____

3

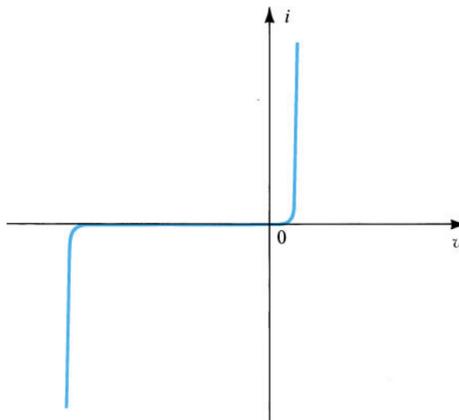


Figure 1: Diode curve.

4.1

Irradiance = _____

4.2

$\lambda =$ _____

4.3

Relative Sensitivity = _____

4.4

Irradiance = _____

5

Current = _____ ; $\lambda =$ _____

6.1

Why do we need the amplifier?

6.2

Receiver 1: $R_f =$ _____ ; $V_{dd} =$ _____

Receiver 2: $R_f =$ _____ ; $V_{dd} =$ _____

6.3

Why is LED in receiver 1 flipped?

6.4

Which configuration is preferred?

7.1

Receiver 1: BW = _____

Receiver 2: BW = _____

7.2

Schematic:

Plot:

Receiver 1: BW = _____

Receiver 2: BW = _____

7.3

BW = _____

What is the effect of a third stage on bandwidth?